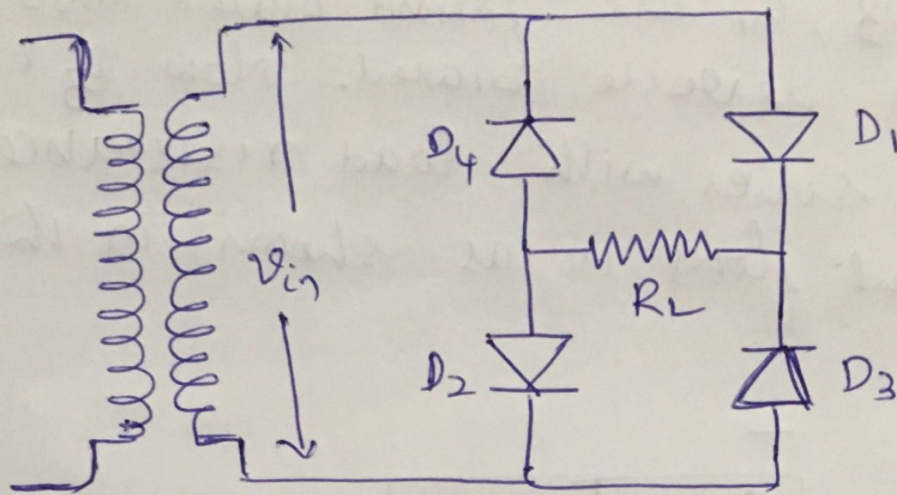


Bridge Rectifier


The fig shows the circuit diagram of full wave bridge rectifier. let the input voltage to the transformer Rectifier be

$$V_{in} = V_m \sin(\omega t)$$

$$0 \leq \omega t \leq 2\pi$$



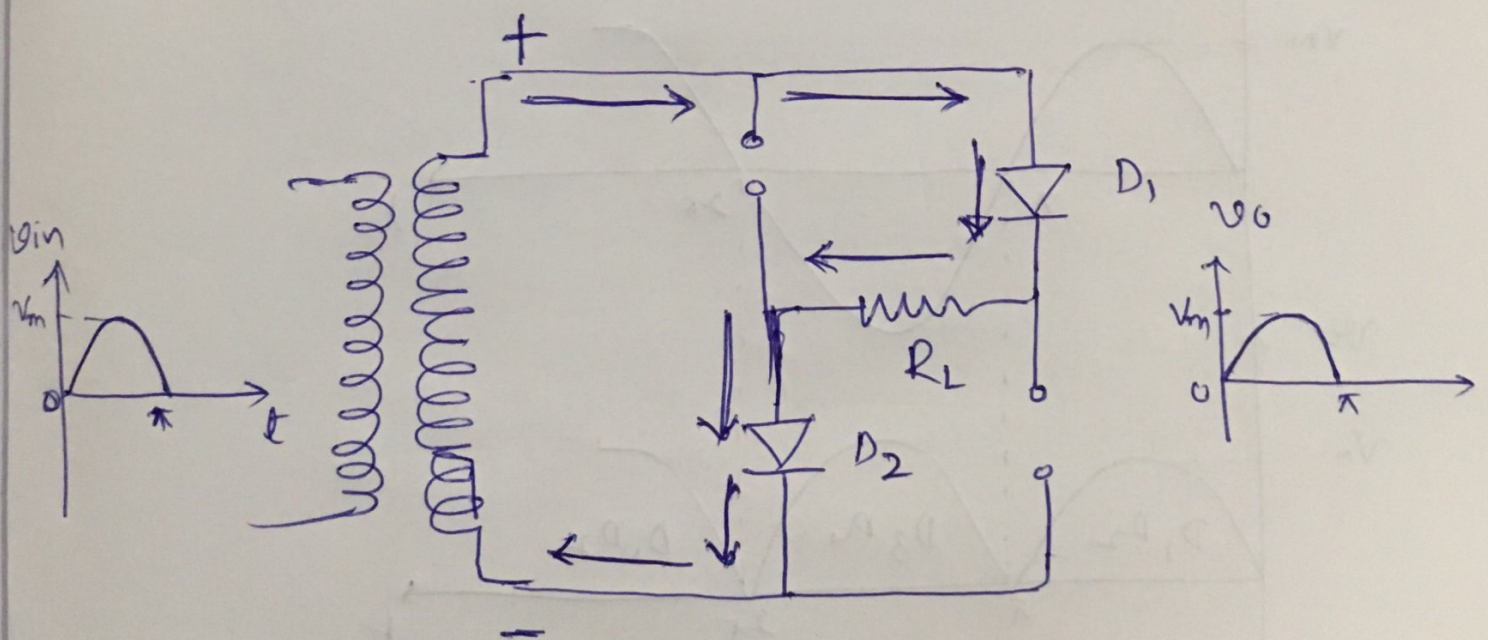Operation of the circuit \rightarrow During the positive half cycle of the input voltage the diode D_1 & D_2 are forward biased, while the diode D_3 & D_4 are reverse biased. The two diode D_1 & D_2 conducts in series with the load & is shown in the figure



During Alternate half cycle of the input voltage the Diode D_3, D_4 are forward biased while Diode D_1 & D_2 are reverse biased. Now D_3 & D_4 conduct in series with load resistance R_L & the current flows is as shown in the figure

