
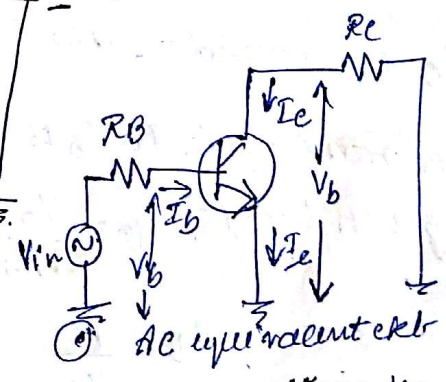
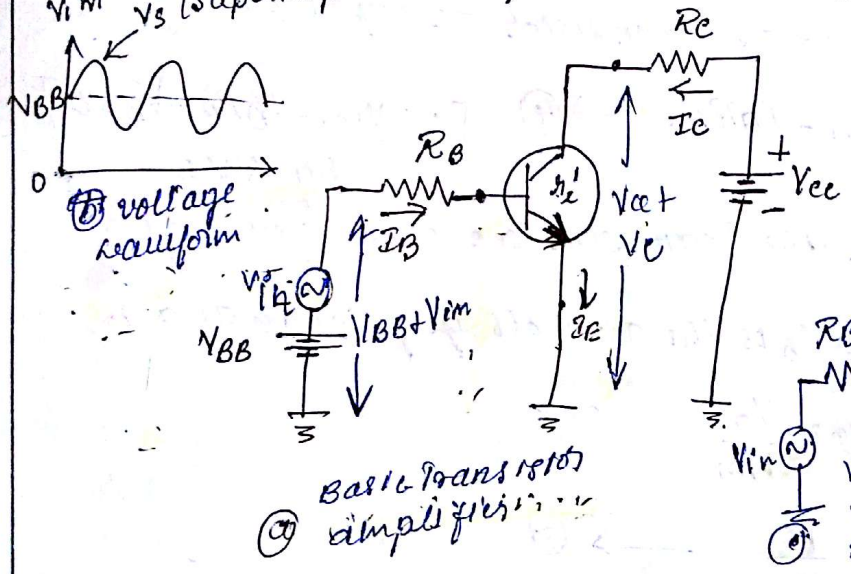
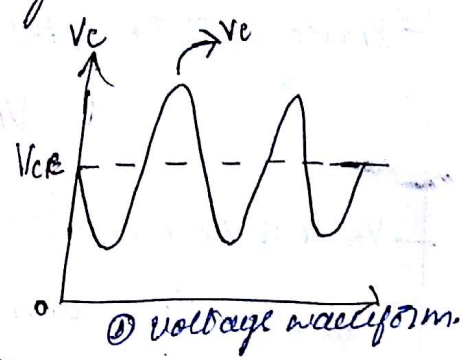


① BJT as an Amplifier

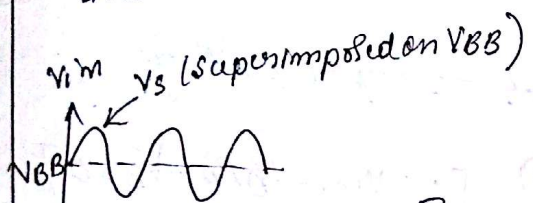- + Amplification: is the process of linearly increasing the amplitude of an electrical signal.
- + A transistor amplifies current because the collector current is equal to the base current multiplied by the current gain β (i.e. $I_c = \beta I_b$). The base current is very small compared to the collector and emitter current.



- fig shows basic amplifier with ac source voltage V_s is superimposed on the dc bias voltage V_{BB} . The dc bias voltage V_{BB} is connected to base through the resistor R_B & the dc bias voltage V_{CC} is connected to collector through resistor R_C . AC equivalent can be represented by making $V_{BB} = 0$ & $V_{CC} = 0$.
- The ac input voltage produces an ac base current, which results in larger ac collector current.
 - The ac collector current produces an ac voltage across R_C , thus producing an amplified but inverted reproduction of ac input voltage in active region.
 - The forward biased emitter-base junction presents a local resistance to the ac signal. This internal ac emitter resistance is designated as $r_{e'}$.

The ac emitter current is given by

$$I_e \approx I_c = \frac{V_b}{r_{e'}} \quad (1) \quad r_{e'} = \frac{V_b}{I_e} \approx \frac{V_b}{I_c} \rightarrow (1)$$

The ac collector voltage V_c equal to the ac voltage drop across R_c ,

$$\therefore V_c = I_c R_c \rightarrow (2)$$

Since $I_e \approx I_c$, the ac collector voltage is given by,

$$V_c \approx I_e R_c \rightarrow (3)$$

V_b can be considered as transistor's ac input voltage

$$\text{where, } V_b = V_{in} - I_b R_B \rightarrow (4) \quad [\because V_{in} - I_b R_B - V_b = 0] \text{ by KVL}$$

V_c considered as the transistor's ac output voltage.

The ratio of V_c to V_b is the ac voltage gain A_v and is given by, $\therefore A_v = \frac{V_o}{V_{in}}$

$$A_v = \frac{V_c}{V_b} \rightarrow (5)$$

we have,

$$V_b = I_e r_{e'} \text{ [from (1)]}$$

$\rightarrow (6)$

where $r_{e'}$ is ac emitter resistance.

substituting eqs. (3) & (6) in (5)

$$A_v = \frac{V_c}{V_b} \approx \frac{I_e R_c}{I_e r_{e'}}$$

\therefore Ac voltage gain

$$A_v \approx \frac{R_c}{r_{e'}} \rightarrow (7)$$

eq (7) shows that transistor provides amplification in the form of voltage gain which is independent of R_c & $r_{e'}$


$\therefore R_c$ is always greater than $r_{e'}$, the o/p voltage V_c is always greater than i/p voltage V_b .

current gain $A_i = I_c / I_b = \beta$ $\therefore I_c \gg I_b$ $\therefore \beta$ is large



power gain $A_p = A_v \cdot A_i$ — product of voltage gain & current gain.

BJT as a Switch

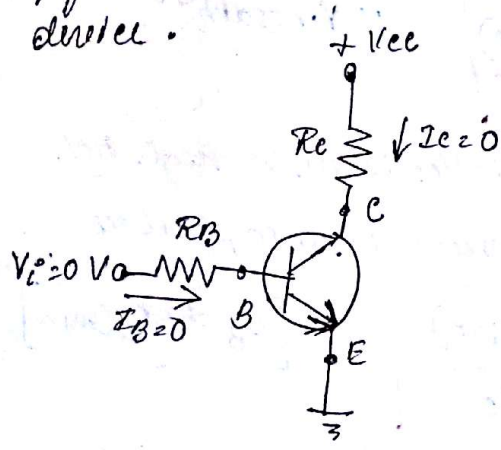
- Second major application area of BJT is switching applicatⁿ.
- When used as an electronic switch, a BJT is normally operated alternately in cut-off & saturation.
- Fig illustrates the basic operation of transistor as a switching device.



(a) cut-off - open switch

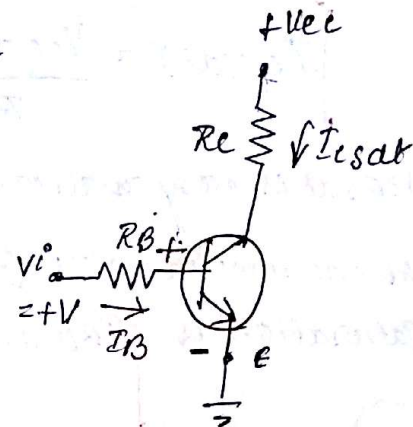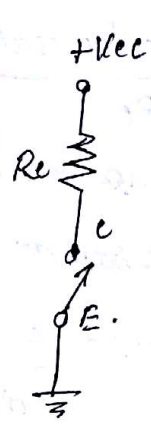

(b) saturation - closed switch

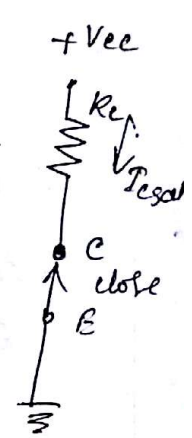

- (a) The transistor is in cut-off region because the BE junction is reverse biased. Hence, there is ideally an open between collector & emitter.
- (b) i.e. when $V_i = 0$, BE junction is reverse biased & transistor is in cut-off region. In this condition, $I_B = I_C = 0$ and there is an open b/w collector and emitter.
- (c) when $V_i = +V$, emitter-base junction is forward biased & base-collector junction are also forward biased. In this condition base current flows & it is greater than I_C / β (to reach its saturation value).

Conditions in cut-off

- As transistor is in cut-off region when base-emitter junction is not forward biased, neglecting leakage current, all of currents are zero & V_{CE} is equal to V_{EE} .

$V_{CE}(\text{cutoff}) = V_{EE}$

Conditions in Saturation

- when base-emitter junction is forward-biased and there is enough base current to produce a maximum collector current, the transistor is saturated.

we have the formula for collector saturation current as,

$$I_{C(sat)} = \frac{V_{CC} - V_{CE(sat)}}{R_C} \quad \because V_{CE(sat)} \ll V_{CC}$$

$\therefore V_{CE(sat)}$ is very small compared to V_{CC} it can be neglected.

- The minimum value of base current needed to produce

saturation is $I_{B(min)} = \frac{I_{C(sat)}}{\beta_{DC}} \quad [I_B \gg I_{B(min)}]$

- I_B should be significantly greater than $I_{B(min)}$ to ensure transistor is operated in saturation region.

③ Transistor switch circuit to switch ON/OFF an LED

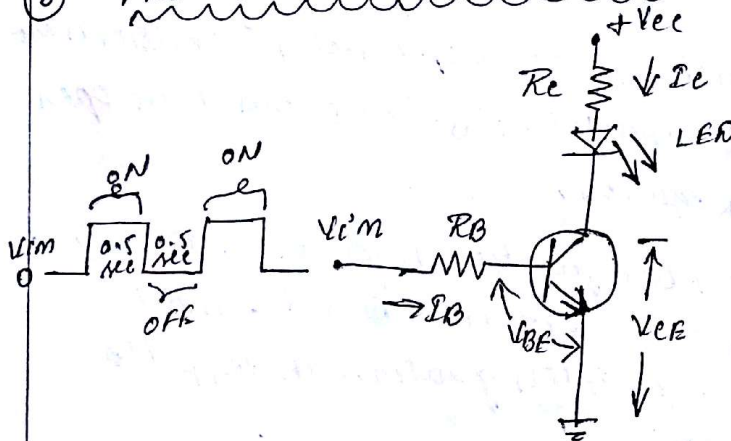


fig ③

fig shows how transistor is used as a switch to turn off & turn on LED.

- A square wave input voltage with a period of 1ms (0.5ms on time & 0.5ms off-time) is applied to the input


- when square wave is at 0V, the base emitter junction is reverse biased and the transistor is in cut-off. As a result, collector current I_c is zero and hence LED does not emit light.
- when square wave goes high, the BE junction is forward biased & there is enough base current to operate the transistor in saturation.
- As a result, collector current I_c flows & it forward biases the LED. The resulting I_c through LED causes it to emit light.
- Thus the LED is on for 0.5 sec & off for 0.5 sec.

Circuit


④ Relay Switch using BJT.

Draw & Explain working of relay switch circuit using BJT to open Turn OFF / ON lamp.

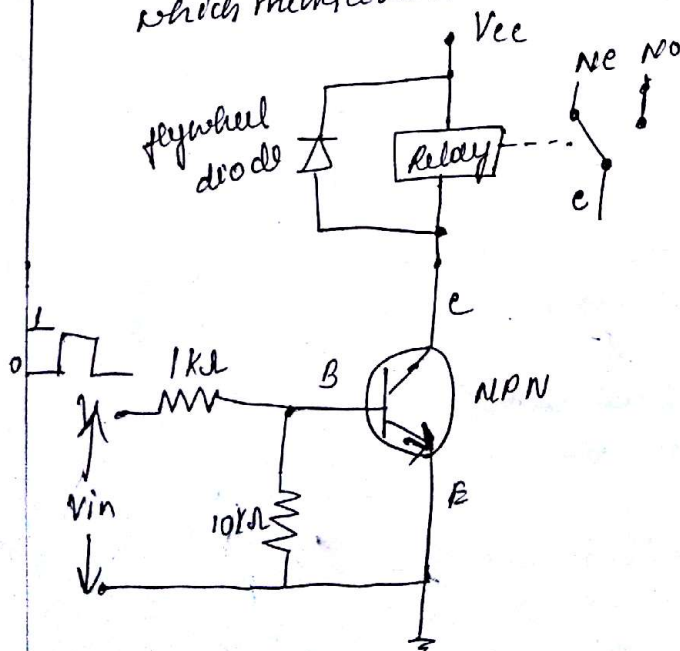- Relays are electromechanical devices that use an electromagnet to operate a pair of movable contacts from an open position to a closed position.
- The advantage of relays is that it takes a relatively small amount of power to operate relay coil, but the relay itself can be used to control motors, heaters, lamps or ac circuits which themselves can draw a lot more electrical power.



Relay Switch circuit

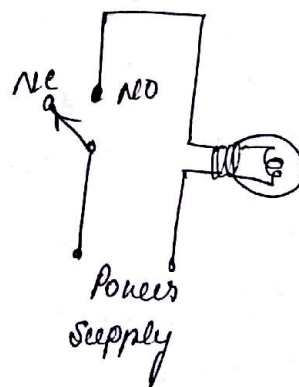

Lamp circuit

Fig @ shows a typical relay switch ckt. The circuit has the coil driven by NPN transistor switch, depending on input voltage level. When base voltage of transistor is zero, the transistor is cut-off & acts as open switch. As a result no collector current flows & the relay coil is de-energised. In this condition, NC (normally closed) contact remains close & normally open contact remains open.

- when base voltage of transistor is sufficient enough to drive transistor in saturation, it acts as closed switch.
- I_c flows & relay coil is energised.
- NC contact gets open & NO normally open contact gets close.

Relationship between α & β

β_{dc} : The dc current gain of the Transistor is the ratio of the dc collector current (I_C) to the dc base current (I_B) i.e.

$$\beta_{dc} = \beta_{dc} = \frac{I_C}{I_B}$$

α_{dc} : The ratio of dc collector current (I_C) to the dc emitter current (I_E) is

$$\alpha_{dc} = \alpha_{dc} = \frac{I_C}{I_E}$$

$\therefore I_C < I_E$. α_{dc} is unity

$$\alpha_{dc} = \frac{I_C}{I_E} = \frac{I_E - I_B}{I_E} = 1 - \frac{I_B}{I_E}$$

We know that $I_E = I_C + I_B$

$$\Rightarrow I_B = I_E - I_C$$

$$\beta_{dc} = \frac{I_C}{I_B} = \frac{I_C}{I_E - I_C}$$

dividing numerator & denominator of RHS of above eqⁿ by I_E

we get,

$$\beta_{dc} = \frac{I_C/I_E}{I_E/I_E - I_C/I_E}$$

$$\Rightarrow \boxed{\beta_{dc} = \frac{\alpha_{dc}}{1 - \alpha_{dc}}}$$

$$\therefore \alpha_{dc} = \frac{I_C}{I_E}$$

N. k.T $\alpha_{dc} = \frac{I_C}{I_E}$ and $I_E = I_B + I_C$

$$\alpha_{dc} = \frac{I_C}{I_B + I_C}$$

dividing num^r & denominator of RHS of above eqⁿ by I_B , we get

$$\alpha_{dc} = \frac{I_C/I_B}{I_B/I_B + I_C/I_B} \Rightarrow \boxed{\alpha_{dc} = \frac{\beta_{dc}}{1 + \beta_{dc}}}$$

$$\therefore \beta_{dc} = \frac{I_C}{I_B}$$