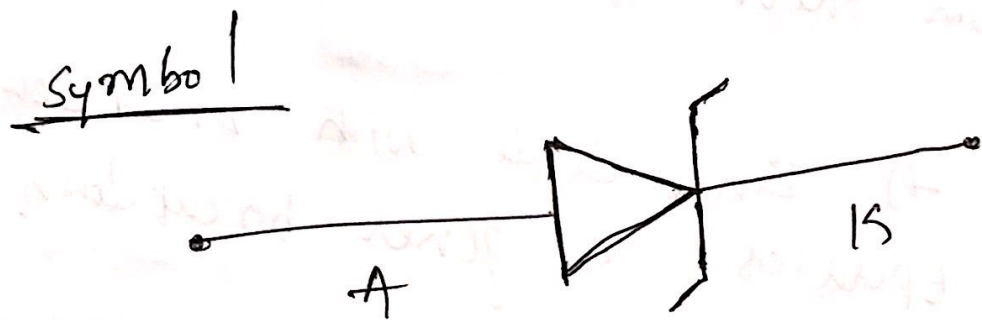


Zener Diode

The zener diode is a silicon pn junction device that is designed to operate in the reverse-breakdown region. the breakdown voltage of a zener diode is set by the doping level during manufacturing.



Operation \Rightarrow

In forward bias the Zener diode operates same as normal diode. In reverse bias a small current flows thro' the diode & is called reverse saturation current. At a certain reverse voltage the reverse breakdown occurs & current through the Zener diode increases rapidly that voltage is called Zener voltage $[V_Z]$.


Zener Breakdown :-

Zener diodes are designed to operate in reverse breakdown. Two types of breakdown in Zener diode are Zener & avalanche breakdown. Where Zener breakdown occurs in Zener diode at low reverse voltages. A Zener diode is heavily doped to reduce the breakdown voltage. This causes a very thin depletion region. As a result, an intense electric field exists in the depletion region. Near the Zener breakdown voltage (V_Z) the electric field is intense enough to pull the electrons from their valence band & creates current.

A Zener diode with breakdown less than 5V operates in Zener breakdown. Those with


breakdown voltage greater than 5V operates in avalanche breakdown.

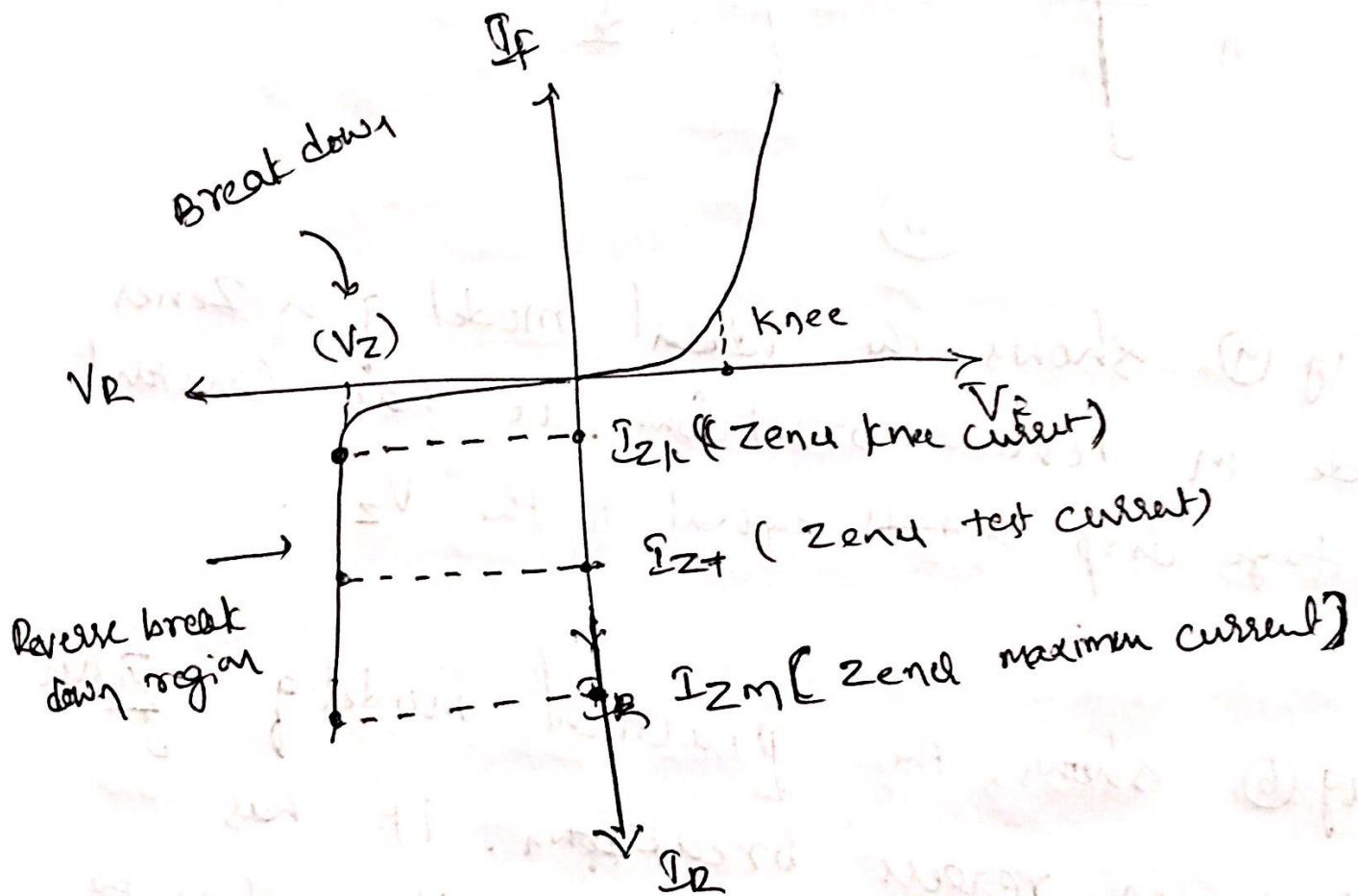The $V-I$ characteristics of Zener Diode is as shown below.




Zener equivalent circuit

Ideal

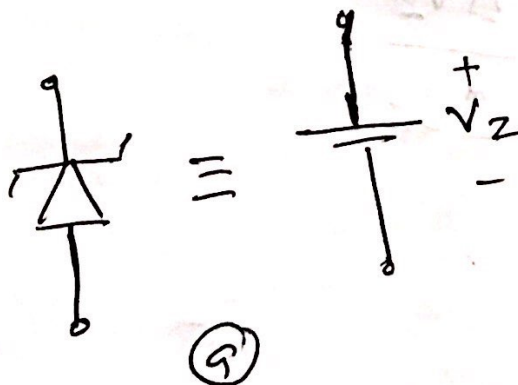

① practical

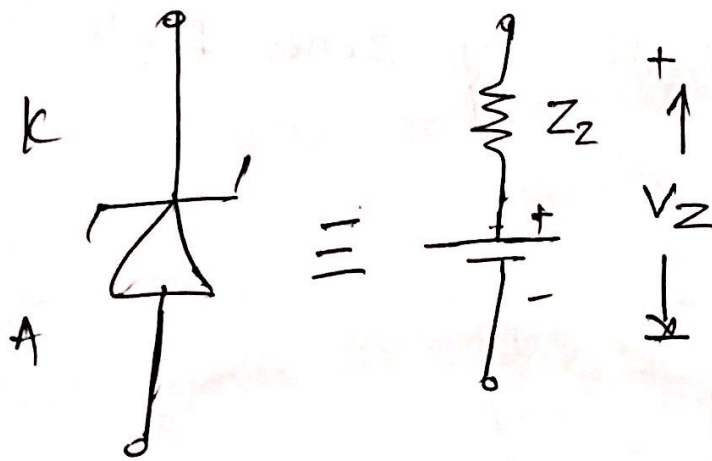


⑥

Fig ⑥ shows the ideal model of a Zener diode in reverse breakdown. it has constant voltage drop ~~across~~ equal to the " V_z ".

Fig ⑥ shows the practical model of a Zener diode in reverse breakdown. it has Zener impedance & constant voltage drop.

$$Z_z = \frac{\Delta V_z}{\Delta I_z}$$

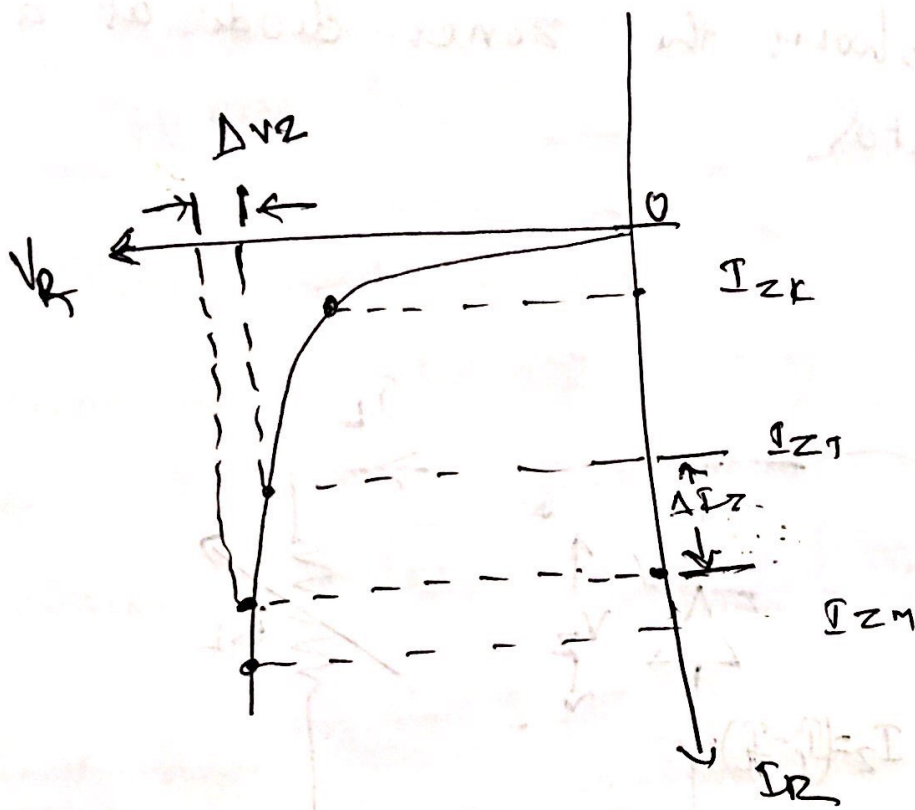


Zener Diode as voltage regulator

The Zener Diode can be used as a type of voltage regulator for providing a stable reference voltage.


Voltage regulators are the device used to maintain a constant voltage across the load despite of fluctuations in the input voltage and load current. The Zener diode in its reverse bias region is widely used as a voltage regulator & continues to operate as with I_{Zmin} & I_{Zmax} .

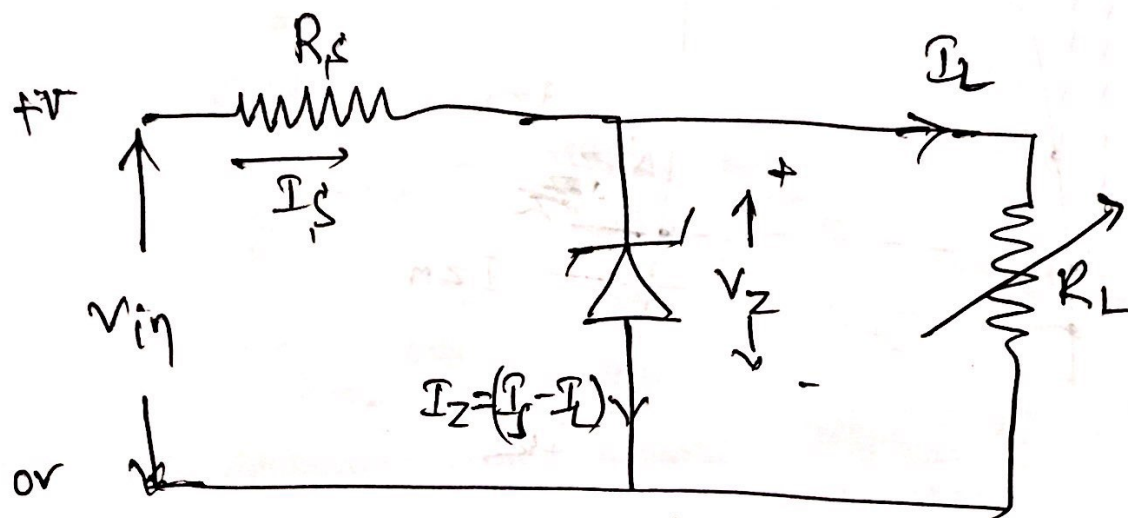The figure shows the zener diode as a voltage regulator



Case - 1 :- when no load is connected ($I_L = 0$)

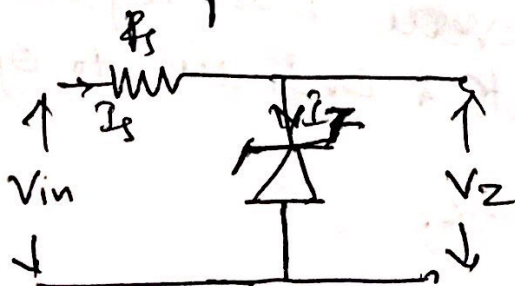
The current flowing in the circuit entirely passes through the zener diode, the diode dissipates maximum power. Thus worst-case must be taken while selecting the series resistance so as to maintain the power dissipation within the range of maximum power dissipating capability of the diode.



$$I_Z = \frac{V_{in} - V_Z}{R_s}$$

Case-II:- When load resistance R_L is connected across the diode.

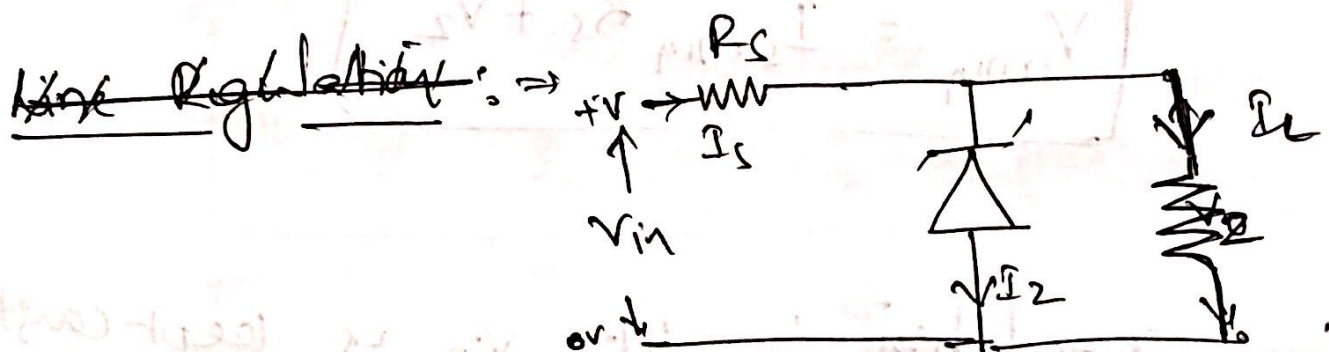Since load is connected in parallel with Zener diode, the o/p voltage will be equal to V_Z . the Zener current must always be above $I_{Z(\min)}$ & below $I_{Z(\max)}$ [max. power rating]



$$I_S = \frac{V_{in} - V_Z}{R_S} = I_Z + I_L$$

$$I_S = I_Z + I_L$$

line regulation \Rightarrow In this case series resistance (R_s) & R_L load resistance are kept constant, & all the variation arises due to the input voltage fluctuation.

$$V_{\text{imax}} = I_{\text{max}} R_s + V_Z$$

$$V_{\text{imin}} = I_{\text{min}} R_s + V_Z$$

load regulation \therefore Let V_{in} is kept constant & load resistance R_L is varied, the variation of R_L changes the current I_L thro' it.

When load resistance R_L increases the load current I_L decreases, this causes increase in the zener current (I_Z) as result the voltage across the diode remains constant

$$R_{L\text{max}} = \frac{V_Z}{I_{L\text{min}}} = \frac{V_Z}{I_s - I_{Z(\text{max})}}$$

$$I_{L(\min)} = \frac{V_{Z}}{R_{L(\max)}} = \frac{V_Z}{R_{L(\max)}}$$

When load resistance (R_L) decreases the load current increases. This causes Zener current (I_Z) to decrease. As a result voltage across Zener diode is maintained constant.

$$R_{L(\min)} = \frac{V_Z}{I_{L(\max)}} = \frac{V_Z}{I_S - I_{Z(\min)}}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}}$$

Related formulas

$$I_{Z(\min)} = I_S - I_{L(\max)} = \frac{V_{\min} - V_Z}{R_S} - I_{L(\max)}$$

$$I_{Z(max)} = I_S - I_{L(min)} = \frac{V_{i(max)} - V_Z}{R_S} - I_{L(min)}$$

$$R_{S(min)} = \frac{V_i - V_Z}{I} \quad V_{i(max)}$$

$$R_{S(min)} = \frac{V_{i(min)} - V_Z}{I_{Z(max)} + I_{L(min)}}$$

$$R_{S(max)} = \frac{V_i - V_Z}{I}$$

$$R_{S(max)} = \frac{V_{i(max)} - V_Z}{I_{Z(min)} + I_{L(max)}}$$