

## Introduction of BJT.

Shruthi H. Shetty  
Asst Professor, ELE  
SCEM regulates

A transistor is a 3 terminal semiconductor device that generates current or voltage flow & acts as a switch or gate of signals.

### Uses of transistor:



- Transistor acts as an amplifier, when signal strength has to be increased.
- Transistor acts as a switch to choose between available options.
- Transistor also regulates the incoming current & voltage of signal.

### Construction

- Transistor is a three terminal device which is formed by connecting two diodes back to back. Hence it has got two PN junctions.
- three terminals are drawn out of 3 semiconductor materials present in it. This type of connection offers two types of transistor.

→ PNP Type

→ NPN Type.

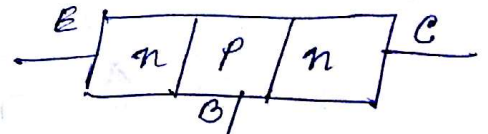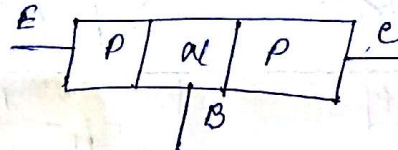

- Three terminals are Emitter (E), Base (B), Collector (C).

### Emitter:

- The left hand side of above fig shows emitter terminal.
- This has a moderate size & is heavily doped as its main function is to supply a number of majority carriers, i.e. either  $e^-$  or holes.
- As this emits electrons, it is called as emitter - E.

### Base:



- The middle material in above figure is Base - B.
- This is thin & lightly doped.
- main function is to pass the majority carriers from the emitter to the collector.

### Collector:

- The right side material in above fig is collector - C.
- The name implies its function of collecting the carriers.
- This is a bit larger in size than emitter & base.
- moderately doped.



## Symbols.

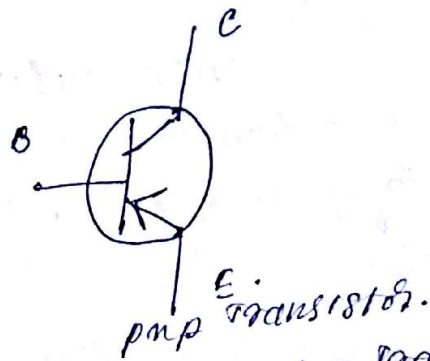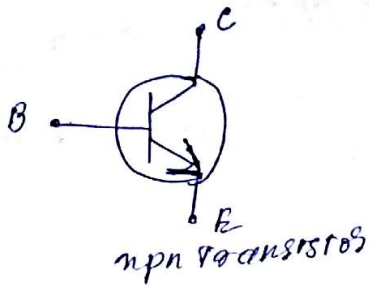





as shown here in figure indicated as emitter of a transistor. As collector of a transistor has to dissipate much greater power it is made large. Due to specific functions of emitter & collector, they are not interchangeable.

- Transistor has 2 junctions

- Emitter Base Junction  $E_B$  - collector Base Junction.

Biasing is controlling the operation of ckt by providing power supply.

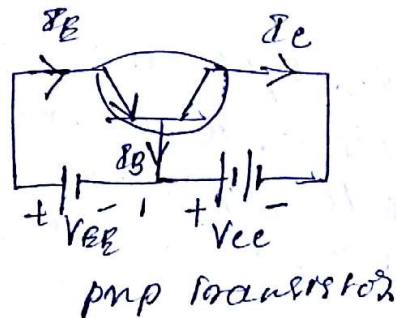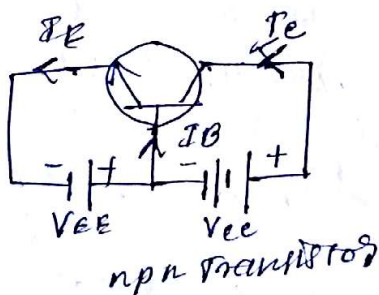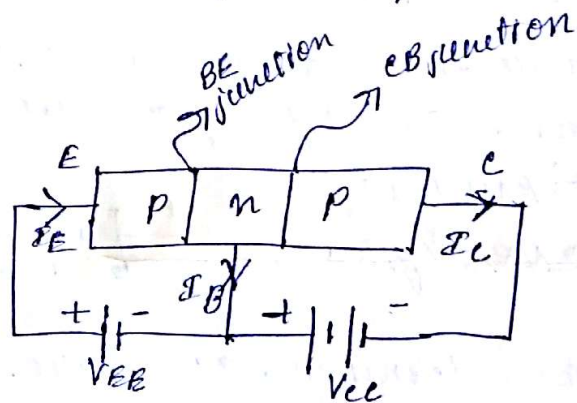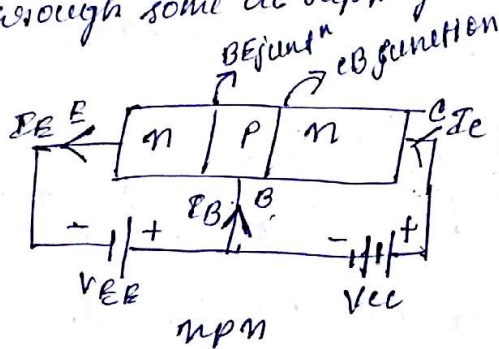- The function of both PNP & NPN is controlled by providing bias to ckt through some dc supply.



- The n-type material is provided negative supply & p-type material is given positive supply to make ckt forward bias.

- The p-type material is provided positive supply & n-type material is given negative supply to make ckt reverse bias.


- By applying power, the emitter base junction is forward biased as emitter resistance is small. - collector base junction is reverse biased as its resistance is bit higher. A small forward bias is sufficient as BE junction whereas high reverse bias has to be applied at collector-base junction.



the direction of current in circuit indicates the conventional current is the movement of holes current which is opposite of electron current.

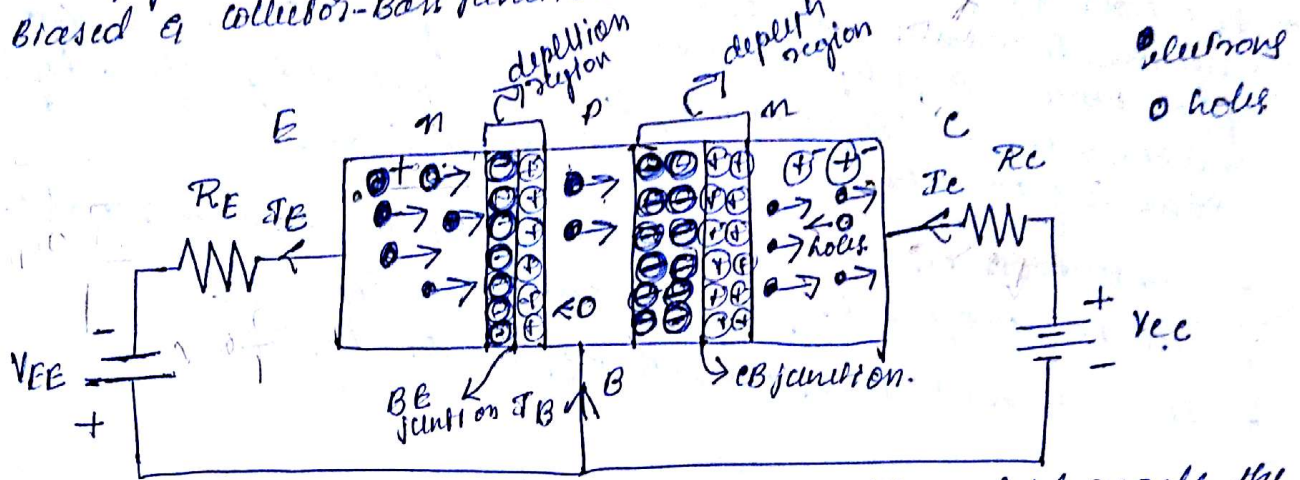
### operation of NPN transistor

- The fig is as shown, in which emitter-base junction is forward biased & collector-base junction is reverse biased.



- $V_{EE}$  provides a negative potential at the emitter which repels the electrons in the n-type material across the emitter-base junction, to reach the base region. A very low percent of electrons recombine with free holes of p region. This provides very low current which constitutes base current  $I_B$ . Remaining holes across the collector-base junction to constitute the collector  $I_C$ .
- As electrons reach out collector terminal, & enter the positive terminal of battery, an electron from negative terminal of battery  $V_{EE}$  enters emitter region.
- conduction of NPN transistor takes place through electrons.
- collector current is higher than emitter current.
- increase or decrease of  $I_E$  current affects the  $I_C$

### operation of PNP

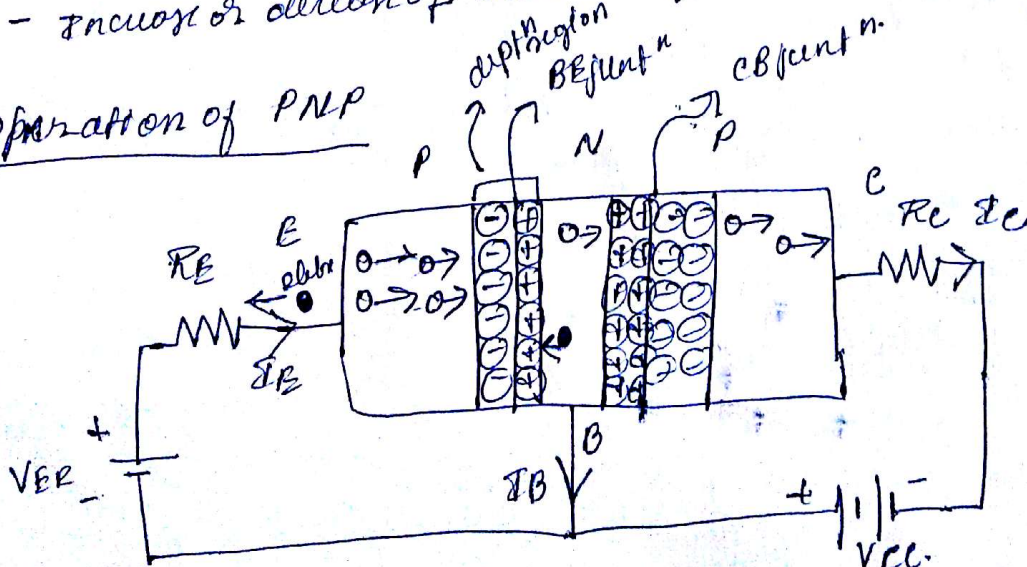



- The voltage  $V_{BE}$  provides positive potential at emitter which repels holes in p-type E then holes cross the E-B junction, to reach B and recombine with free electrons of N region.
- This provides low current  $-I_B$ . Remaining holes cross the EB junction to constitute  $I_E$ , which is hole current.
- As a hole reaches the collector terminal, an electron from the battery's negative terminal fills space in collector. This flow slowly increases  $I_E$  electron minority current flow through emitter. When each electron entering the +ve terminal of  $V_{BE}$  is replaced by a hole by moving towards emitter junction. This constitutes  $I_E$ .
- Conduction in PNP transistor takes place through holes.
- collector current is slightly less than  $I_E$ .
- Energy dissipation in  $I_E$  affects the  $I_E$ .

### Advantages of Transistor.

- high voltage gain.
  - low supply voltage is sufficient.
  - Most suitable for low power applications.
  - smaller & lighter in weight.
  - mechanically stronger than vacuum tubes.
  - very suitable to integrate with resistors & diodes to produce IC's.
- There are few disadvantages such as they cannot be used for high power applications due to lower power dissipation. They have lower input impedance & they are temperature dependent.





## Transistor Configuration

- Transistor has 3 terminals emitter, base, collector. Using these 3 terminals, transistor can be connected in a ckt with one terminal common to both i/p & o/p in 3 different possible configurations.
- 3 types of configuration.
  - common base
  - common emitter
  - common collector.

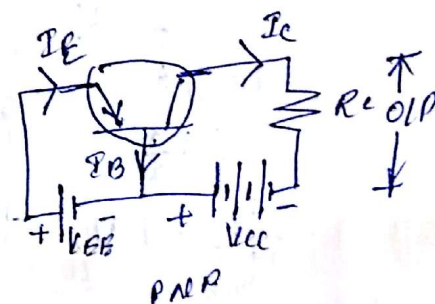
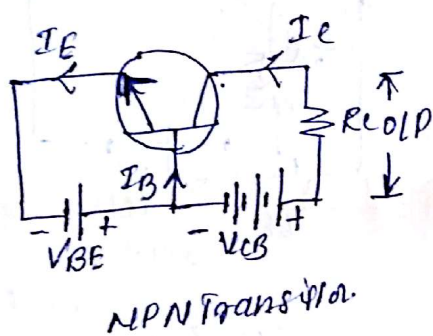
### Common Base Configuration

- Base terminal is taken as common terminal for both input & output of transistor.
- The common base connection for NPN is as shown.





### Characteristics

- provides voltage gain but no current gain.
- Keeping  $V_{EB}$  constant, with a small increase in  $V_{EB}$ ,  $I_E$  gets increased.
- $I_E$  is independent of  $V_{CB}$
- $R_i = \Delta V_{EE} / \Delta I_E$  |  $V_{CB} = \text{constant}$        $R_o = \frac{\Delta V_{CE}}{\Delta I_C}$  | at  $I_E \text{ constant}$
- $V_{CB}$  can affect  $I_C$  only at low voltages when  $V_{EB}$  is constant.
- $R_i$  is low, a small value of  $V_{EB}$  is enough to produce large  $I_E$ .
- $R_o$  is high, large  $V_{CB}$  change produces a little  $I_C$ .
- configuration provides good stability against temperature.
- used for high frequency applications.

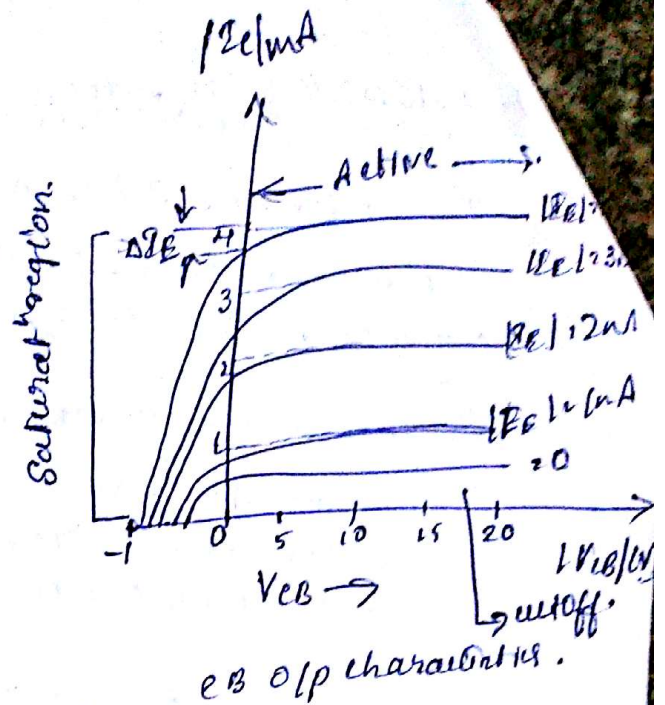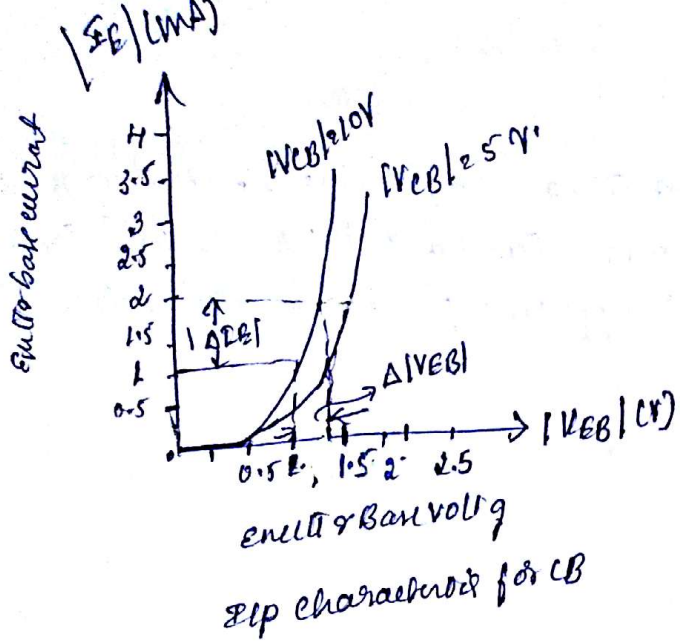



### Common emitter configurations

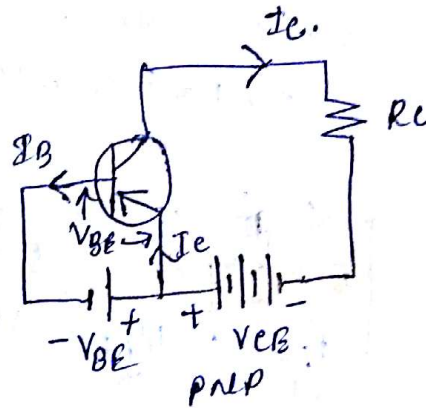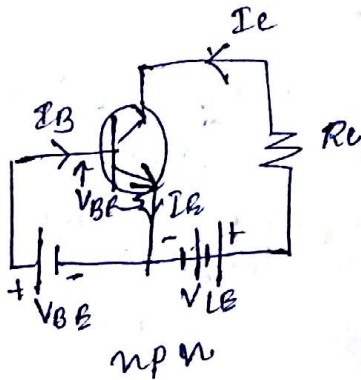


### characteristics

- configuration provides good current gain & voltage gain.
- keeping  $V_{CE}$  constant with small increase in  $V_{BE}$ ,  $I_B$  increases rapidly.
- $I_C \approx \beta I_B$  for any value of  $V_{CE}$  above knee voltage.
- $R_i = \frac{\Delta V_{BE}}{\Delta I_E} \bigg|_{V_{CE} = \text{const}}$  is low, hence small  $V_{BE}$  enough to produce large  $I_B$
- $R_o = \frac{\Delta V_{CE}}{\Delta I_C} \bigg|_{I_B = \text{const}}$  is less than that of CB ckt
- used for bias stabilization networks & audio frequency applications.




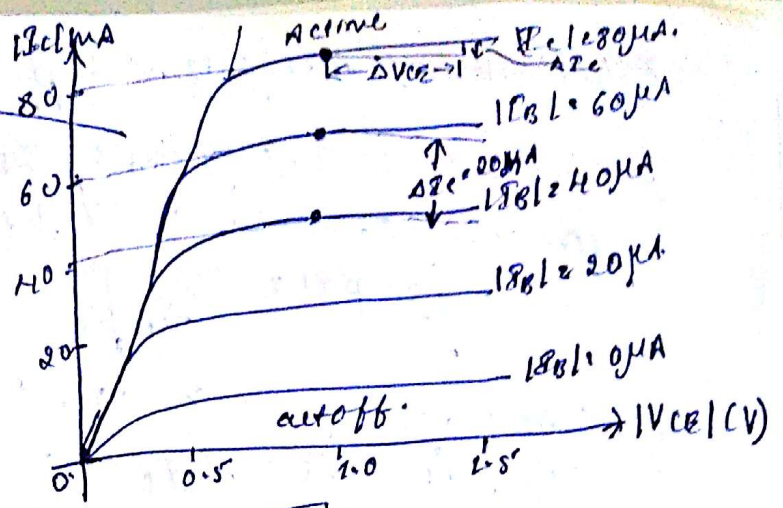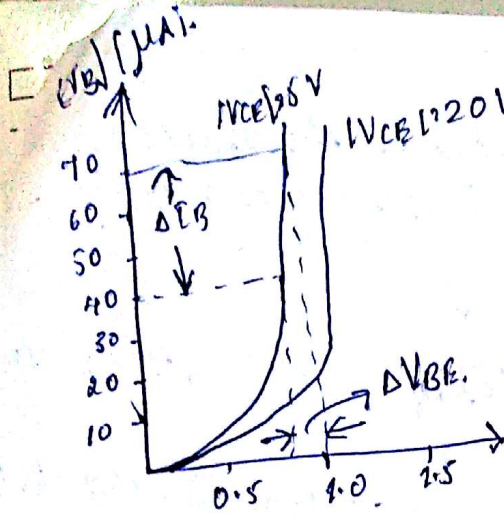

Common collector

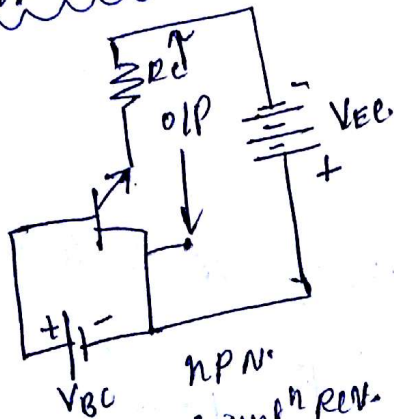

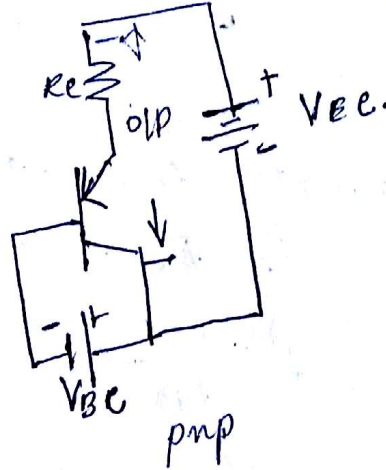$E_{out} \approx E_{in}$  &  $E_{out} \approx E_{in}$



Characteristics

- provides current gain but no voltage gain
- $I_P$  resistance is high &  $O/P$  resistance is low
- voltage gain provided by this ckt is less than 1
- $I_E + I_B = I_C$
- $I_P$  &  $O/P$  signals are in phase.
- works as non inverting amplifier.
- is mostly used for impedance matching. to drive low impedance load from high impedance source.